

AC time $\rightarrow$ phasor (sinusoidal domain)

$$\cos a \cos b = \frac{1}{2}(\cos(a+b) + \cos(a-b))$$
$$\cos(a+b) = \cos a \cos b - \sin a \sin b$$

L's $\perp$ lags V

Gen. sin. $v(t) = V_m \cos(\omega t + \phi) = V_m \cos \phi \cos \omega t - V_m \sin \phi \sin \omega t$

$$v'(t) = \omega V_m \cos(\omega t + \phi + 90^\circ) \rightarrow j\omega X$$

$$\int v(t) dt = \frac{1}{\omega} V_m \cos(\omega t + \phi - 90^\circ) \rightarrow \frac{1}{j\omega} X$$

E. sin excitation $\rightarrow y(t) = y_F(t) + y_N(t)$

$$y_F(t) = A \cos \omega t + B \sin \omega t \quad y_N(t), \text{ turn source off, w/i.v.}$$

Stable lin. circuit $\rightarrow$ sin steady state, same ω

Cmplx $j r \angle \theta = r \angle (\theta + 90^\circ)$

Phasor $v(t) = V_m \cos(\omega t + \phi) \leftrightarrow \underline{V} = V_m \angle \phi$ ω lost!

$$= |\underline{V}| \cos(\omega t + \angle \underline{V})$$

Rotating phasor $\underline{V} = V_m \angle \phi$


$$\underline{V} e^{j\omega t} = V_m e^{j(\phi + \omega t)}$$
$$= \underline{V_m \cos(\omega t + \phi)} + j V_m \sin(\omega t + \phi)$$
$$v(t) = \text{Re}(\underline{V} e^{j\omega t})$$

If $\text{Re}(\underline{V}_A e^{j\omega t}) = \text{Re}(\underline{V}_B e^{j\omega t}) \quad \forall t, \leftrightarrow \underline{V}_A = \underline{V}_B$

sum if $\sum_{i=1}^N V_{m_i} \cos(\omega t + \phi_i) = V_m \cos(\omega t + \phi)$

$$\sum_{i=1}^N \underline{V}_i = \underline{V}$$

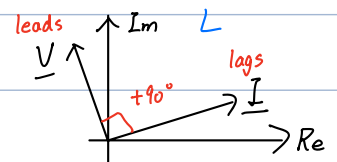Impedance $\underline{I} = I_m \angle \phi_I, \underline{V} = V_m \angle \phi_V$ $\underline{Z} \equiv \frac{\underline{V}}{\underline{I}}$



R $v(t) = R i(t) \rightarrow \underline{V} = R \underline{I}$

$\underline{I} = G \underline{V}$ (same $\angle$)

L $v(t) = L \frac{di(t)}{dt} \rightarrow \underline{V} = j\omega L \underline{I}$

$\underline{I} = \frac{1}{j\omega L} \underline{V}$ (+90° $\rightarrow$ left shift $\rightarrow$ lead) (v leads by 90, i lags)

C $v(t) = \frac{1}{C} \int i(t) dt \rightarrow \underline{V} = \frac{1}{j\omega C} \underline{I}$

$\underline{I} = j\omega C \underline{V}$ (v lags by 90)

$$\underline{Z} \equiv R + jX$$

R: resistance; X: reactance = $\text{Im}(\underline{Z})$

Admittance $\underline{Y} \equiv \frac{1}{\underline{Z}} = \frac{\underline{I}}{\underline{V}} = G + jB$

G: conductance; B: susceptance


$$G = \frac{R}{R^2 + X^2} \neq \frac{1}{R} \quad B = -\frac{X}{R^2 + X^2} \neq -\frac{1}{X}$$

KVL $\sum_n v_n(t) = 0 \rightarrow \sum_n \underline{V}_n = 0$

KCL $\sum_n \underline{I}_n = 0$

Dep. source same thing, same unit (real const.)

Source trans. $\underline{Z}_p = \underline{Z}_s, \underline{I}_s = \frac{V_s}{\underline{Z}_s}$

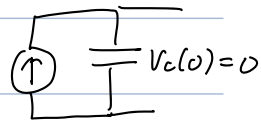Pathological E. no sin steady state, $V_c = 0$ forces a DC, ^{w/o R} never dies out! 

E. RF wire inductance $\rightarrow$ balance w/ $\frac{1}{\omega C} = \omega L$ in series (resonance)

Node-V $\underline{I} = \frac{V_x - V_y}{\underline{Z}}$

Mesh-I $\underline{V} = \underline{Z}(\underline{I}_x - \underline{I}_y)$

Superposition 1. All indep. same ω ✓

2. diff. ω ?? $\rightarrow$ $\underline{Z}$ differ from sources $\rightarrow$ find $(t) \rightarrow$ add

Thevenin $\underline{V}_{oc}$ series w/ $\underline{Z}_{Th}$

Norton $\underline{I}_{sc}$ parallel

$\underline{I}_{sc} \underline{Z}_{Th} = \underline{V}_{oc}$

Active same thing, just with $\underline{Z}_I$ E. i.: $\frac{V_o}{V_i} = -\frac{\underline{Z}_F}{\underline{Z}_I}$


1. Opamp gain $\downarrow$ at high ω ! (large internal C for stability)

2. DC feedback path!

E. AC coupled amp, C filters DC

$\frac{V_o}{V_i} = -\frac{\underline{Z}_F}{\underline{Z}_I} = -\frac{R_F}{R_i + \frac{1}{j\omega C}} \approx -\frac{R_F}{R_i}$ for $\frac{1}{\omega C} \gg R_i$


$C \gg \frac{1}{\omega R_i}$ (large)

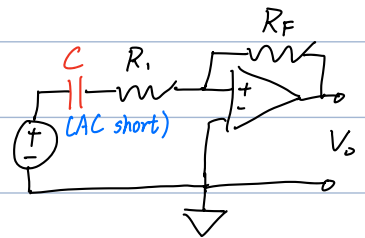

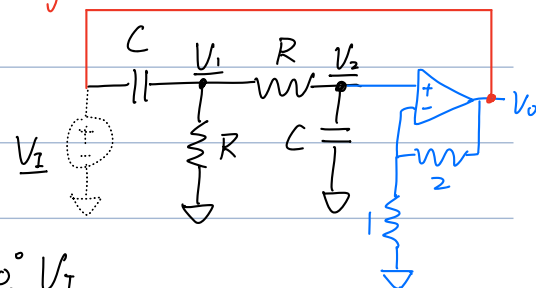E. Feedback oscillator $\frac{V_1 - V_2}{1/j\omega C} + \frac{V_1}{R} + \frac{V_1 - V_2}{R} = 0$
 $\frac{V_1 - V_2}{R} = \frac{V_2}{1/j\omega C}$

$\underline{V}_2 = \frac{j\omega RC}{(1 - \omega^2 R^2 C^2) + j3\omega RC} \underline{V}_1$

$\underline{V}_2$ real when $\omega = \frac{1}{RC} \equiv \omega_0 \rightarrow \underline{V}_2 = \frac{1}{3} \angle 0^\circ \underline{V}_1$ where



Then use n.i. amp to amplify back $3\times$. $\rightarrow$ feedback as $\underline{V}_2$, self-driven

AC power

instantaneous $p(t) = v(t) i(t)$ (passive)

avg $\overline{p(t)} \equiv P = \frac{1}{T} \int_0^T p(t) dt$

Prop. $\overline{k f_1(t) + f_2(t)} = k \overline{f_1(t)} + \overline{f_2(t)}$

$$\overline{\cos(\omega t + \phi)} = 0$$

$$\overline{\cos^2(\omega t + \phi)} = \frac{1}{2}$$

same ϕ !
 $\overline{\sin(\omega t + \phi) \cos(\omega t + \phi)} = 0$ ($\sin x \cos x = \frac{1}{2} \sin 2x$)

rms $P = \overline{i^2(t) R} = (\overline{i^2(t)}) R \rightarrow I_{rms} \equiv \sqrt{\overline{i^2(t)}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$
 $= I_{rms}^2 R$

$$V_{rms} = I_{rms} R \xrightarrow{\text{ana}} DC$$

$P \equiv P_{avg}$ is NOT P_{rms} !

E. sinusoid

$$i(t) = I_m \cos(\omega t + \phi)$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

R v/i in phase $p(t) = V_m I_m \cos^2(\omega t) = \frac{1}{2} V_m I_m (1 + \cos(2\omega t))$

$$P = \frac{1}{2} V_m I_m = V_{rms} I_{rms}$$

L i lags v

$$p(t) = V_m \cos(\omega t) I_m \cos(\omega t - 90^\circ) = \frac{1}{2} V_m I_m \sin(2\omega t)$$

$$P = 0 \text{ (avg.)}$$

C i leads v

$$p(t) = - \cos(\omega t) \sin(\omega t + 90^\circ) = -\frac{1}{2} \sin(2\omega t)$$

$$P = 0 \text{ (avg.)}$$

General $p(t) = v(t) i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$ $\cos x \cos y = \frac{1}{2} [\cos(x-y) + \cos(x+y)]$

$$= \frac{1}{2} V_m I_m [\cos(\theta_v - \theta_i) + \underbrace{\cos(2\omega t + \theta_v + \theta_i)}_{\text{avg} = 0}]$$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$i(t) = I_m \cos(\omega t + \theta_i) \Rightarrow I_m \angle \theta_i$$

$$= I_{m1} \angle \theta_v + I_{m2} \angle \theta_v - 90^\circ$$

proj. in-phase $\Rightarrow I_m \cos(\theta_v - \theta_i) \cos(\omega t + \theta_v)$ quadrature $I_m \sin(\theta_v - \theta_i) \sin(\omega t + \theta_v)$

$$p(t) = v(t) i(t) = V_m \cos(\omega t + \theta_v) [I_{m1} \cos(\omega t + \theta_v) + I_{m2} \sin(\omega t + \theta_v)]$$

$$= V_m I_{m1} \cos^2(\omega t + \theta_v) + V_m I_{m2} \cos(\omega t + \theta_v) \sin(\omega t + \theta_v)$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) [1 + \cos(2\omega t + 2\theta_v)] + \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \sin(2\omega t + 2\theta_v)$$

$\rightarrow P \rightarrow$ average power

$\rightarrow Q \rightarrow$ reactive power (borrow/return)

[VAR]

Apparent power $\underline{P} = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$ $S \equiv V_{rms} I_{rms}$ [VA]

power factor $P = S \cdot pf$, $pf \equiv \cos(\theta_v - \theta_i)$


↳ How efficiently avg. power is absorbed

pf. angle $\equiv \theta_v - \theta_i$ (lag/lead), lost in cos

Complex power $\underline{S} = S \angle \theta_v - \theta_i$, $|\underline{S}| = S = V_{rms} I_{rms}$
 $= P + jQ$

$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$ $Q = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$

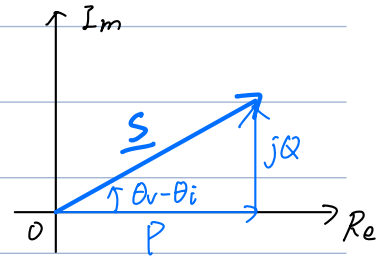$\underline{S} = V_{rms} I_{rms} \angle \theta_v - \theta_i = V_{rms} \angle \theta_v I_{rms} \angle -\theta_i = V_{rms} I_{rms}^*$



where $\underline{V}_{rms} \equiv V_{rms} \angle \theta_v$, $\underline{I}_{rms} \equiv I_{rms} \angle \theta_i$

Passive loads $\underline{Z} = \frac{V}{I} = \frac{V_m}{I_m} \angle \theta_v - \theta_i = \frac{V_{rms}}{I_{rms}} \angle \theta_v - \theta_i = \frac{V_{rms}}{I_{rms}}$

$\underline{Z} = R + jX$, same $\angle$ w/ $\underline{S}$

$\underline{S} = I_{rms}^2 \underline{Z} = I_{rms}^2 R + j I_{rms}^2 X$

$I_{rms} = \frac{V_{rms}}{|\underline{Z}|}$

$P = I_{rms}^2 R$, $Q = I_{rms}^2 X$

	R, P	X, Q	$\theta = \theta_v - \theta_i$	pf	($P \geq 0$)
pure R	> 0	0	0	1	
L	≥ 0	> 0	$[0, 90^\circ]$	lag	
pure L	0	> 0	90°	0	
C	≥ 0	< 0	$[-90^\circ, 0)$	lead	
pure C	0	< 0	-90°	0	
active	can < 0				

$\underline{S}$ conservation $\underline{S} = V_{rms} \underline{I}_{rms}^* = V_{rms1} \underline{I}_{rms1}^* + \dots + V_{rmsn} \underline{I}_{rmsn}^* = \underline{S}_1 + \dots + \underline{S}_n$

$\underline{S} = \sum \underline{S}_i$ cons. of complex power

$P = \sum P_i$ avg.

$Q = \sum Q_i$ reactive

pf correction $P = V_{rms} I_{rms} \cdot pf$


$pf = \cos(\theta_v - \theta_i)$

If V_{rms} fixed, $I_{rms} \uparrow$ to compensate pf

E. motor w/ high $L \rightarrow$ add C to correct pf.

$$Q = Q_{load} + Q_c$$

$$= Q_{load} - V_{rms}^2 \omega C$$

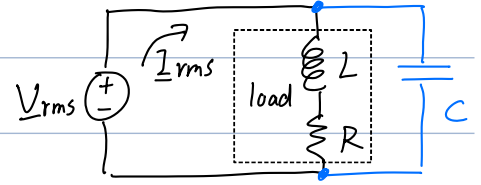

Don't want to over compensate ($pf = 0.95$ good)

Max avg. power transfer given fixed $Z_s = R_s + jX_s$

To max I_{rms} , $I_{rms} = \frac{V_{s,rms}}{|Z|} = \frac{V_{s,rms}}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$ want if $X_L = -X_s$

$\rightarrow$ normal match $\rightarrow P_L = I_{rms}^2 R_L$

$R_L = R_s$

$Z_L = Z_s^*$

* Power is not linear at some ω

if $\omega_1 \neq \omega_2$, $P_1 = \frac{V_{rms1}^2}{R}$, $P_2 = \frac{V_{rms2}^2}{R}$, $P = \frac{V_{rms1}^2}{R} + \frac{V_{rms2}^2}{R} + \frac{2 \overline{v_1(t)v_2(t)}}{R}$ if $\omega_1 \neq \omega_2$

$\hookrightarrow$ Then $P = P_1 + P_2$


3-phase (Y)

$V_{an}(t) = \sqrt{2} V_p \cos(\omega t) \leftrightarrow V_p \angle 0^\circ$

$V_{bn}(t) = \cos(\omega t - 120^\circ) \leftrightarrow V_p \angle -120^\circ$ delay 120°

$V_{cn}(t) = \cos(\omega t - 240^\circ) \leftrightarrow V_p \angle -240^\circ$ delay 240°

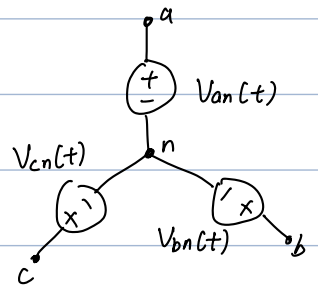Now assume $V_p \equiv V_{rms} = \frac{\text{peak}}{\sqrt{2}}$



$V_{an} + V_{bn} + V_{cn} = 0 \rightarrow \Sigma$ in t also 0.

balanced set. same mag, & differ by 120°

Line-to-line voltage $V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_p \angle 30^\circ \equiv V_L \angle 30^\circ$


V_L : rms of line voltage $V_{bc} = V_L \angle -90^\circ$

$\sqrt{3} V_p$ $V_{ca} = V_L \angle +150^\circ$

$V_{ab} + V_{bc} + V_{ca} = 0 \rightarrow$ also balanced

Balanced Y-Y $\rightarrow$ same $\underline{Z}_Y$ (balanced load)
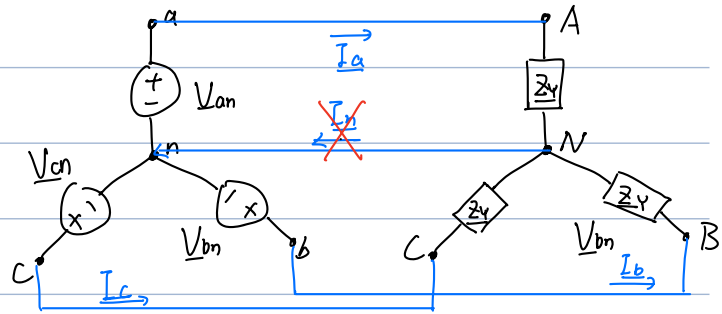
$$\underline{I}_a = \frac{\underline{V}_{an}}{\underline{Z}_Y} \quad \underline{I}_b = \frac{\underline{V}_{bn}}{\underline{Z}_Y} \quad \underline{I}_c = \frac{\underline{V}_{cn}}{\underline{Z}_Y}$$



All $\underline{I}$ rotated by same $(-\angle \underline{Z}_Y) \rightarrow$ balanced

$$I_L = |\underline{I}_a| = |\underline{I}_b| = |\underline{I}_c| = \frac{V_p}{|\underline{Z}_Y|}$$

$\underline{I}_n = \underline{I}_a + \underline{I}_b + \underline{I}_c = 0$ if balanced (not needed, or much thinner wire)


$$p(t) = v_{an}(t) i_a(t) + v_{bn}(t) i_b(t) + v_{cn}(t) i_c(t)$$

$$= 3 V_p I_L \cos \theta$$

$$= \sqrt{3} V_L I_L \cos \theta$$

$$\theta = \angle \underline{Z}_Y$$

(const!)

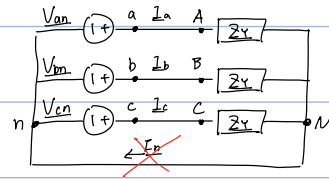


Balanced Y- Δ

$$I_\Delta = |\underline{I}_{AB}| = |\underline{I}_{BC}| = |\underline{I}_{CA}| = \frac{V_L}{|\underline{Z}_\Delta|}$$


$$\underline{I}_a = \underline{I}_{AB} - \underline{I}_{CA}$$
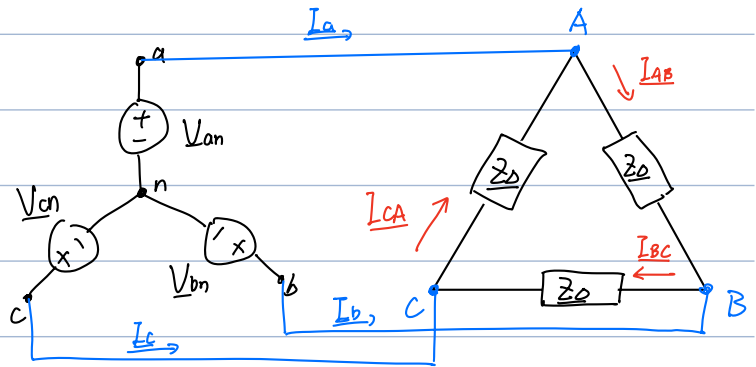
$$\underline{I}_b = \dots, \quad \underline{I}_c = \dots$$



E. home $\underline{Z}_3$ uses 240V rms

Ground on metal parts

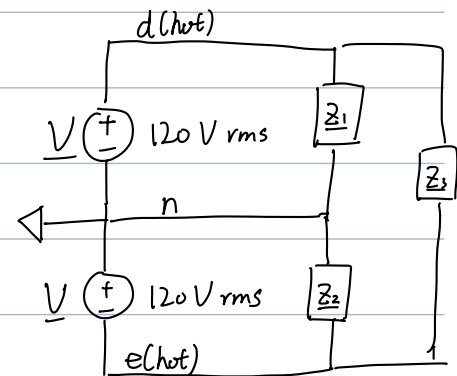

B coupling - share same flux

$$\phi_1 = \alpha N_1 i_1 + k_m \alpha N_2 i_2, \quad 0 \leq k_m \leq 1$$

$$\lambda_1 = N_1 \phi_1 = (\alpha N_1^2) i_1 + (k_m \alpha N_1 N_2) i_2$$

$$\equiv L_1 i_1 + M_{12} i_2$$

$$L_1 \equiv \alpha N_1^2 \quad M_{12} \equiv k_m \alpha N_1 N_2$$

$$M_{12} \equiv M_{21} = M \equiv k_m \sqrt{L_1 L_2}$$

$$W = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

$$v_1(t) = \frac{d\lambda_1}{dt} = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$\underline{V}_1 = j\omega L_1 \underline{I}_1 + j\omega M \underline{I}_2$$

Ideal trans $L_1, L_2 \rightarrow \infty, k=1$

$$\left. \begin{aligned} \frac{V_2}{V_1} &= \frac{N_2}{N_1} = n \\ \frac{i_2}{i_1} &= \frac{N_1}{N_2} = \frac{1}{n} \end{aligned} \right\} v_2(t) i_2(t) = v_1(t) i_1(t)$$

No P consumption or storage for ideal

$$\underline{Z}_{in} = \frac{\underline{Z}_L}{n^2}$$

→ transform $\underline{V}, \underline{I}, \underline{Z}$!

w-response

$$x(t) \rightarrow \boxed{} \rightarrow y(t)$$

$$X_m \cos(\omega t + \theta_x) \rightarrow \boxed{} \rightarrow Y_m \cos(\omega t + \theta_y)$$

$$M(\omega) = \frac{Y_m}{X_m}$$

$$\phi(\omega) = \theta_y - \theta_x$$

$$H(j\omega) = \frac{V}{X}$$

$$V_o / V_i$$

$$= |H(j\omega)|$$

$$= \angle H(j\omega)$$

$$I_o / I_i$$

$$V_o / I_i$$

$$I_o / V_i$$

v. gain


i. gain

transimpedance

transadmittance

$$E. H(j\omega) = \frac{V_o}{V_i} = \frac{1}{1 + j\omega RC}$$
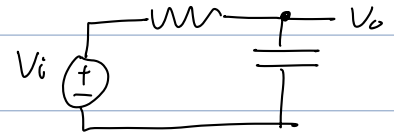
$$M(\omega) = \frac{1}{\sqrt{1 + (\omega RC)^2}}, \quad \phi(\omega) = -\tan^{-1}(\omega RC)$$



Resonant (parallel RLC)

$$\frac{1}{Z} = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

$$Z = \frac{R}{1 + jR(\omega C - \frac{1}{\omega L})}$$

$$|Z| = \frac{R}{\sqrt{1 + R^2(\omega C - \frac{1}{\omega L})^2}}, \quad \angle Z = -\tan^{-1}(R(\omega C - \frac{1}{\omega L}))$$

$$\text{when } \omega = \frac{1}{\sqrt{LC}} \equiv \omega_0, \quad Z = R$$

$$\text{Drive w/ } I_i \rightarrow V_o = Z I_s \rightarrow \text{max output at res!}$$

$$\text{Quality factor } Q \equiv 2\pi \frac{\text{total w stored}}{\text{w stored w/i 1 period}}$$

$$= 2\pi \frac{\frac{1}{2} C V_m^2}{\frac{1}{2} \frac{V_m^2}{R} \frac{2\pi}{\omega_0}}$$

$$Q_0 = R\omega_0 C = R\sqrt{\frac{C}{L}} = \frac{R}{\omega_0 L}$$

$$Q \uparrow \text{ as } R \uparrow$$


$$B \quad \omega \text{ when } |Z| = \frac{|Z_0|}{\sqrt{2}} \quad (\text{half-power})$$

$$\text{here phase shift is } \pm 45^\circ \rightarrow \omega_{1,2} = \omega_0 \sqrt{1 + \frac{1}{4Q_0^2}} \mp \frac{\omega_0}{2Q_0}$$

$$\omega_1 \omega_2 = \omega_0^2$$

$$B = \omega_2 - \omega_1 = \frac{1}{RC} = \frac{\omega_0}{Q_0}$$

$$\text{At resonance, } |I_C| = |I_L| = Q_0 |I_i|$$

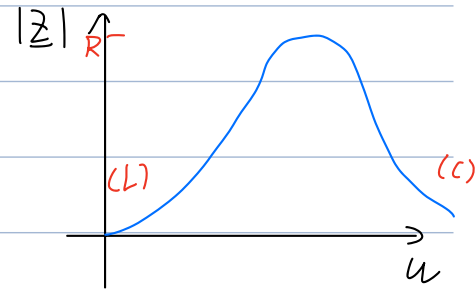

$$L \text{ dominance : } +90^\circ \quad (\angle Z)$$

$$C \quad -90^\circ \quad (\angle Z)$$


Series RLC

$$\underline{Z} = R + j(\omega L - \frac{1}{\omega C}) \quad \underline{I}_0 = \frac{V_i}{\underline{Z}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$B = \frac{R}{L} = \frac{\omega_0}{Q_0}$$

At res, $|V_L| = |V_C| = Q_0 |V_i|$

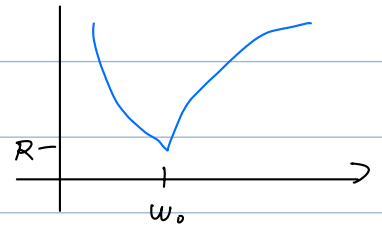

Lossless RLC

|| reject at $\omega = \omega_0$

— pass at $\omega = \omega_0$

Filters

LP, HP, BP, B reject, care about $|H|$

Passive V-div., $H(j\omega) = \frac{V_o}{V_i} = \frac{\underline{Z}_2}{\underline{Z}_1 + \underline{Z}_2}$

Passband at $\omega_p \rightarrow$ make $\underline{Z}_2(j\omega_p) \rightarrow \infty$ or $\underline{Z}_1(j\omega_p) \rightarrow 0$


Stopband at ω_s $\underline{Z}_2(j\omega_s) \rightarrow 0$, $\underline{Z}_1(j\omega_s) \rightarrow \infty$

1st order

E. passive LPF

$$H(j\omega) = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC}$$

cutoff $\omega_c \equiv \frac{1}{RC}$

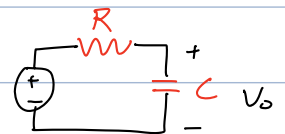

$$M(\omega) = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}} \quad \frac{1}{\sqrt{2}} \text{ at } \omega_c, \quad \phi(\omega) = -\tan^{-1} \frac{\omega}{\omega_c} \rightarrow -90^\circ$$

LR

$$H(j\omega) = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega \frac{L}{R}}$$

$$\omega_c = \frac{R}{L}$$


E. HPF

$$H(j\omega) = \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{1 + j\omega RC} \equiv \frac{j \frac{\omega}{\omega_c}}{1 + j \frac{\omega}{\omega_c}}$$

$$M(\omega) = \frac{\frac{\omega}{\omega_c}}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}} \quad \phi(\omega) = 90^\circ - \tan^{-1} \frac{\omega}{\omega_c}$$

BPF
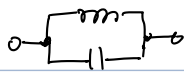
$$\omega = 0 \quad \omega = \omega_0 \quad \omega = \infty$$



$$0$$

$$\infty$$

$$0$$



$$\infty$$

$$0$$


$$\infty$$

E. PBPF

$$H(j\omega) = \frac{R}{R + j\omega L + 1/j\omega C} = \frac{j\omega RC}{1 + j\omega RC + (j\omega)^2 LC}$$

$$\text{cutoff} \equiv \omega_1, \omega_2$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

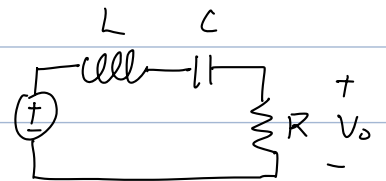

BSF


$$H(j\omega) = \frac{1}{1 + (j\omega)^2 LC} = \frac{1}{1 + (j\omega)^2 RC + (j\omega)^2 LC} \quad (\text{notch filter})$$

E. Audio crossover

E. bypassing, AC coupling to use C to take hi/DC component so the desired go thru load

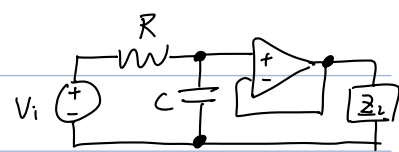E. DC bias + AC signal LDC divider $\xrightarrow{Th} R \Rightarrow V_{AC} - C - R$ analysis)

Active 1. buffering $\underline{Z}_L$ interferes passive components.



E. transconductor to conv. $V \rightarrow I \Rightarrow$ drive || RLC

2. Active filter (in. amp) $\frac{V_o}{V_i} = -\frac{\underline{Z}_2}{\underline{Z}_1}$

E. ALPF $H(j\omega) = -\frac{1}{R_1} \cdot \frac{R_2 \cdot 1/j\omega C_2}{R_2 + 1/j\omega C_2} = -\frac{R_2}{R_1} \frac{1}{1+j\omega R_2 C_2} \equiv \frac{k}{1+j\omega/\omega_c}$





$k \equiv -\frac{R_2}{R_1}$, can > 1 , $\omega_c \equiv \frac{1}{R_2 C_2}$

AHPF $H(j\omega) = k \frac{j\omega/\omega_c}{1+j\omega/\omega_c}$



ABPF can do ALPF — AHPF :

$H(j\omega) = k \frac{j\omega/\omega_{c1}}{(1+j\omega/\omega_{c1})(1+j\omega/\omega_{c2})}$,

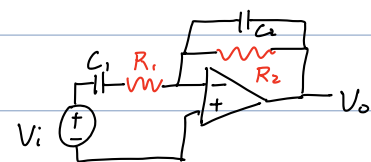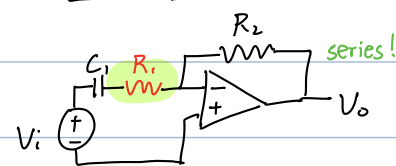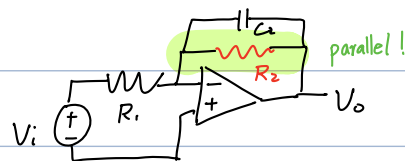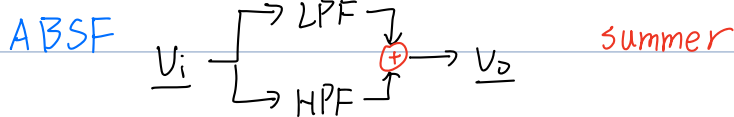broad, need $\omega_{c2} \gg \omega_{c1}$



Pre-emphasis: pass lo/hi f w/ diff. gain

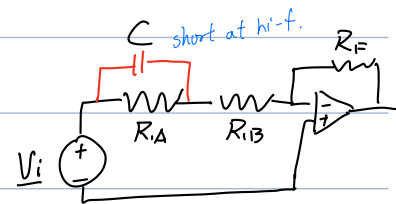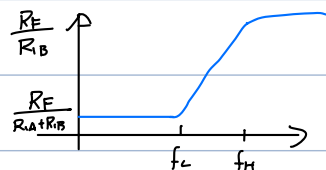

Scaling 1. impedance (RLC) $\underline{Z} \rightarrow k_z \underline{Z}$ $L' = k_z L$, $C' = \frac{1}{k_z} C$

V, I ratios don't change, ω_0, B unchanged

2. frequency $A(j\omega) \rightarrow A'(jk_f \omega)$ $L' = \frac{1}{k_f} L$ $C' = \frac{1}{k_f} C$

$\omega_0' \rightarrow k_f \omega_0$, amp unchanged

Bode plot

- k

- $j \frac{\omega}{\omega_a}$

- $1 + j \frac{\omega}{\omega_a}$

- $1 + 2\zeta(j \frac{\omega}{\omega_a}) + (j \frac{\omega}{\omega_a})^2$

$$b = \frac{2\zeta}{\omega_a} \quad c = \frac{1}{\omega_a^2}$$

Log $\text{dB} = 10 \log\left(\frac{P_z}{P_i}\right) = 10 \log\left(\frac{V_z^2/R}{V_i^2/R}\right)$

$$= 20 \log\left(\frac{V_z}{V_i}\right)$$

$$\sqrt{2} \approx 3 \text{ dB}^{(V)}$$

(cutoff)

$$M_{dB}(\omega) = 20 \log(M(\omega))$$

H^N

$\rightarrow$

M^N

$N \cdot M_{dB}$

$N \cdot \phi$

$H_1 \times H_2$

$\rightarrow$

$M_1 \cdot M_2$

$M_{1,dB} + M_{2,dB}$

$\phi_1 + \phi_2$

1. const. K

$$M_{dB} = 20 \log |K|$$

$$\phi = 0^\circ$$


$$(180^\circ \text{ if } K < 0)$$

2. $j \frac{\omega}{\omega_a}$

$$M_{dB}(\omega_a) = 0$$

$$\phi = 90^\circ (j)$$

+20 dB/decade

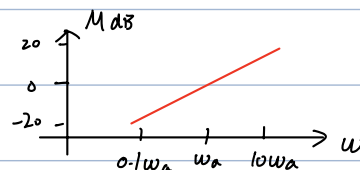

3. $1 + j \frac{\omega}{\omega_a}$

$\approx 1, \omega \ll \omega_a$ } straight line approx. of 1 and 2.

$\approx j \frac{\omega}{\omega_a}, \omega \gg \omega_a$

3 dB at ω_a

0 dB $\rightarrow$ lin +20 dB/dec ; $0^\circ \rightarrow$ lin +45°/dec $\rightarrow 90^\circ$

$$M_{dB}(\omega) = 20 \log \sqrt{1 + \left(\frac{\omega}{\omega_a}\right)^2} \quad \phi(\omega) = \tan^{-1}\left(\frac{\omega}{\omega_a}\right)$$

4. $1 + 2\zeta(j \frac{\omega}{\omega_a}) + (j \frac{\omega}{\omega_a})^2$

$$\approx 1, \omega \ll \omega_a$$

$$0 \text{ dB}$$

$$0^\circ$$

$$\approx (j \frac{\omega}{\omega_a})^2, \omega \gg \omega_a$$

$$40 \text{ dB/dec}, 180^\circ$$

bad at $\omega \approx \omega_a$, especially for low ζ , since $H(j\omega_a) \approx 0$

ϕ sharper at low ζ

M_{dB}, ϕ add / $\cdot N$

Opamp gain

A $\downarrow$ at hi- ω . Also phase shift $\rightarrow$

$$V_o = \frac{A(j\omega)}{A_o} V_D$$

$$= \frac{1}{1 + j \frac{\omega}{\omega_b}} V_D$$

$\omega = A_o \omega_b$: unity gain freq.

Complex ω

$$v(t) = V_m e^{\sigma t} \cos(\omega t + \phi) \quad \text{exp factor}$$

$$= \text{Re} \{ \underline{V_m} e^{j\phi} e^{(\sigma + j\omega)t} \} \quad s \equiv \sigma + j\omega$$

$$= \text{Re} \{ \underline{V} e^{s t} \}$$

$$= \text{Re} \{ \underline{V} e^{s t} \}$$

$\omega < 0$, same (cos even)

$$x(t) = e^{\sigma t} X_m \cos(\omega t + \phi_x) \rightarrow \boxed{} \rightarrow y(t) = e^{\sigma t} Y_m \cos(\omega t + \phi_y)$$

$$\underline{X} = X_m \angle \phi_x \rightarrow \boxed{H(s)} \rightarrow \underline{Y} = Y_m \angle \phi_y$$

E. L , $i(t) = \text{Re}(\underline{I} e^{s t})$

$$v(t) = L \frac{di}{dt} = \text{Re}(s L \underline{I} e^{s t}) = \text{Re}(\underline{V} e^{s t}) \quad (\underline{V} = s L \underline{I} \text{ ana. } j\omega L \underline{I})$$

$$\underline{V} = \frac{1}{s} \underline{I}$$

Def. Generalized imp $\underline{Z} = \frac{\underline{V}}{\underline{I}}$ ($R, sL, \frac{1}{sC}$), behavior under $|s|$

$$\underline{H}(j\omega) = \underline{H}(s) |_{s=j\omega}$$

3D plot to show $|\underline{H}(s)|$, σ , ω (prev. we've only looked $\sigma=0$, $\omega \geq 0$)


General $\underline{H} = \frac{\underline{Y}}{\underline{X}} = \frac{P(s)}{Q(s)} = \underline{K_H} \frac{(s-z_1) \dots (s-z_m)}{(s-p_1) \dots (s-p_n)} \rightarrow \text{zero}$

E. $\underline{H}(s) = \frac{s}{s+4} = \frac{s-0}{s-(-4)} \quad \begin{matrix} z=0 \\ p=-4 \end{matrix}$

$$\underline{H}(j\omega) = \frac{j\omega-0}{j\omega-(-4)} \quad (\text{length ratio, } \angle \text{ diff})$$

$$|\underline{H}(j\omega)| = |\underline{K_H}| \frac{r_1 \dots r_m}{l_1 \dots l_n}$$
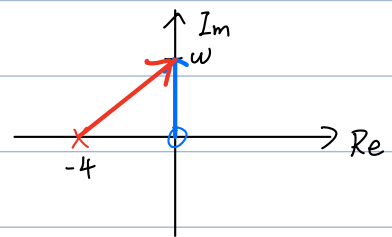
$$\angle \underline{H}(j\omega) = \angle \underline{K_H} + r_1 + \dots + r_m - l_1 - \dots - l_n$$



Complex excitation

$$\underline{x}(t) \rightarrow \boxed{} \rightarrow \underline{y}(t)$$

$$\underline{X} e^{s t} \longrightarrow \underline{Y} e^{s t}$$

$$\text{Re}[\underline{x}(t)] \rightarrow \rightarrow \text{Re}[\underline{y}(t)]$$

DFQ



$\underline{H}(s)$

$$x^{(k)}(t) = s^k \underline{X} e^{s t}$$

$$a_n y^{(n)} + \dots + a_0 y = b_m x^{(m)} + \dots + b_0 x$$

$$(a_n s^n + \dots + a_0) \underline{Y} e^{s t} = (b_m s^m + \dots + b_0) \underline{X} e^{s t}$$

$$\underline{H}(s) = \frac{\underline{Y}}{\underline{X}} = \frac{b_m s^m + \dots + b_0}{a_n s^n + \dots + a_0}$$

Natural $a_n y_n^{(n)} + \dots + a_0 y_n = 0$

$$(a_n \lambda^n + \dots + a_0) A e^{\lambda t} = 0$$

$$y_n(t) = A e^{\lambda_1 t} + \dots + A_n e^{\lambda_n t}$$

$$\text{Let } y_n(t) = A e^{\lambda t}$$

roots: λ

(if complex, must be conj.)

$H(s)$ poles are natural freqs. except in cancellation


on circuit: deactivate source. Diff. circuits may have same natural w.

Stability (natural dies out?)

only p matter. z don't.

LT convert circuit to s-domain + init. cond.

3-terminal network E. K

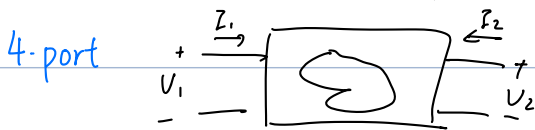

admittance / impedance / hybrid params.